

Possibly Useful Information:  $\mu_0 = 4\pi \times 10^{-7} \text{ N/A}^2$   $e = 1.60 \times 10^{-19} \text{ C}$

**Problem 1** Multiple Choice (3 points each)

\_\_\_\_\_ [i] What is the direction of the force on a vertical wire with an upward current in the earth's magnetic field? (a) north (b) south (c) east (d) west (e) up (f) down (g) cannot be determined


\_\_\_\_\_ [ii] A particle moves in a clockwise (when viewed from above) circle in a downward pointing constant magnetic field. What charge does the particle have? (a) positive (b) negative (c) zero (d) magnetic charge (e) cannot be determined

\_\_\_\_\_ [iii] Three  $4\Omega$  resistors are connected in series across a 24V battery. What is the power dissipated in each resistor? (a) 16W (b) 48W (c) 144W (d) 432W (e) none of the listed (f) cannot be determined

**Problem 2**

(a) Complete the table with the current through and the voltage across each resistor in the circuit. (8 points)


	$100\Omega$	$120\Omega$	$150\Omega$
V			
I			

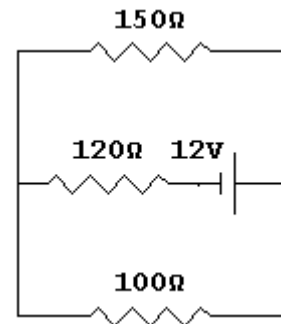


(b) What is the force on an alpha particle (2 protons and 2 neutrons) with a velocity of  $\langle 2, -3, -1 \rangle \times 10^6 \text{ m/s}$  in a magnetic field of 8 mT in the negative z-direction? (6 points)

**Problem 3** (6 points each)


(a) What is  $V_b - V_a$ ?

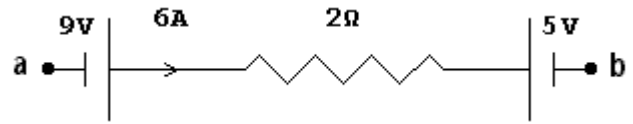

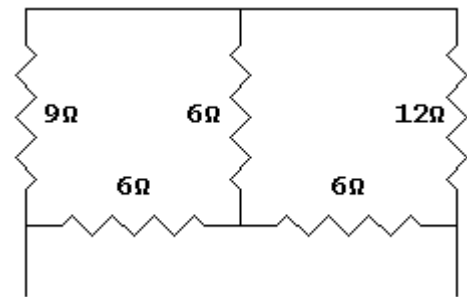(b) What is the equivalent resistance of the combination shown?



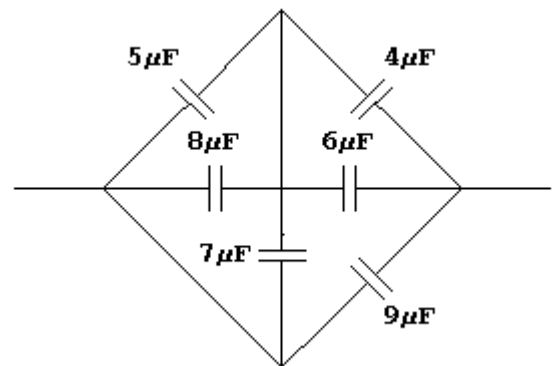(c) What is the equivalent capacitance of the combination shown?



**Problem 4** A copper wire with a 3mm diameter is connected across a battery. At 20°C a 6A current flows through the wire. At 20°C:  $\rho_{\text{copper}} = 1.7 \times 10^{-8} \Omega \cdot \text{m}$  and  $\alpha_{\text{copper}} = 0.0039/\text{C}^\circ$

(a) What is the electric field inside the wire? (6 points)

(b) If the temperature is increased to 50°C then what is the current through the wire, assuming the battery's voltage remains constant? (6 points)

**Problem 5** When an empty parallel-plate capacitor with a cross sectional area of  $3 \times 10^{-4} \text{m}^2$  is connected across 50V, 5nC of charge flows to each plate. (6 points each)

(a) What is the separation of the plates?

(b) How much energy is stored in this capacitor?