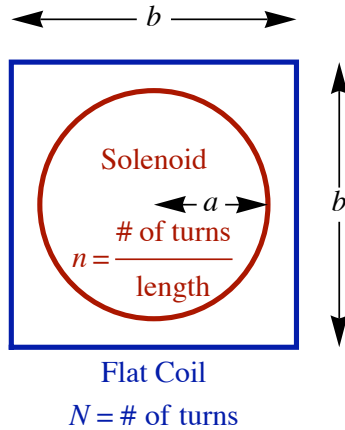


Chapter H - Problems

Blinn College - Physics 2426 - Terry Honan

Problem H.1

Refer to **Problem G.9** where a $b \times b$ square flat coil with N turns sits outside of a long solenoid with n turns per length and a circular cross-section radius a . What is the mutual inductance between the solenoid and the flat coil?



Solution to H.1

In **Problem G.9** we had the induced EMF in the flat coil as


$$\mathcal{E}_2 = -N \mu_0 n \pi a^2 \frac{dI_1}{dt}$$

where I am now referring to the EMF in the coil as \mathcal{E}_2 . Using the definition of mutual inductance

$$\mathcal{E}_2 = -M \frac{dI_1}{dt} \implies M = N \mu_0 n \pi a^2.$$

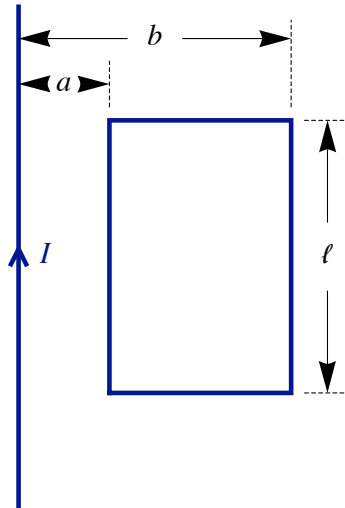Problem H.2

Refer to **Problem G.7** where we discussed a long wire next to a rectangular conduction loop. What is the mutual inductance between the long wire and the loop?



Solution to H.2

We saw in Problem G.7 that

$$\mathcal{E} = -\frac{d\Phi}{dt} = -\frac{\mu_0 \ell}{2\pi} \ln \frac{b}{a} \times \frac{dI}{dt}.$$

Take the current of the long wire to be I_1 and the induced EMF in the loop to be \mathcal{E}_2 then use the definition of mutual inductance:

$$\mathcal{E}_2 = -M \frac{dI_1}{dt} \text{ and } \mathcal{E}_2 = -\frac{\mu_0 \ell}{2\pi} \ln \frac{b}{a} \times \frac{dI_1}{dt} \implies M = \frac{\mu_0 \ell}{2\pi} \ln \frac{b}{a}.$$

Problem H.3

What is the average induced EMF when the current through a coil with a 50 mH inductance varies from 5 A to 3 A in 0.04 s?

Solution to H.3

$$|\bar{\mathcal{E}}| = L \left| \frac{\Delta I}{\Delta t} \right| = 0.050 \times \frac{2}{0.04} = 2.5 \text{ V}$$

Problem H.4

The current through a 15 mH inductor varies as

$$I(t) = I_{\max} \sin \omega t \text{ where } I_{\max} = 6 \text{ A and } \omega = 200 \text{ s}^{-1}.$$

What is the EMF across the inductor as a function of time?

Solution to H.4

$$\begin{aligned}\mathcal{E} &= -L \frac{dI}{dt} = -L \frac{d}{dt} I_{\max} \sin \omega t = -L \omega I_{\max} \cos \omega t \\ &= -0.015 \times 200 \times 6 \cos \omega t = -(18 \text{ V}) \cos[(200 \text{ s}^{-1}) t]\end{aligned}$$

Problem H.5

A solenoid has 250 turns, a length of 40 cm and a diameter of 3 cm. The current through the solenoid varies as

$$I(t) = 15 t^3 - 40 t + 30 \quad (\text{in SI units}).$$

- (a) What is the inductance of the solenoid?
 (b) What is the voltage drop across the solenoid at $t = 2$ s?
 (c) What is the energy stored in the solenoid at $t = 2$ s?

Solution to H.5

- (a) This is a long solenoid. The inductance of a long solenoid is:

$$L = \mu_0 \frac{N^2}{\ell} A = 4\pi \times 10^{-7} \frac{250^2}{0.40} (\pi 0.015^2) = 1.3879 \times 10^{-4} = 0.139 \text{ mH}$$

- (b) The voltage drop is $V = L dI/dt$. We need to differentiate the current.

$$\begin{aligned}\frac{dI(t)}{dt} &= 45 t^2 - 40 \implies \frac{dI}{dt}(2) = 45 \times 2^2 - 40 = 140 \\ \implies V &= L \frac{dI}{dt} = L \times 14 = 0.0194 \text{ V}\end{aligned}$$

- (c) The energy stored in an inductor is $U = \frac{1}{2} L I^2$.

$$I(2) = 15 \times 2^3 - 40 \times 2 + 30 = 70 \implies U = \frac{1}{2} L I^2 = \frac{1}{2} L \times 70^2 = 0.340 \text{ J}$$

Problem H.6

A typical electric field at the earth's surface is 100 V/m and a typical magnetic field value is $5 \times 10^{-5} \text{ T}$. What are the electric and magnetic energy density, u_e and u_m .

Solution to H.6

$$u_e = \frac{1}{2} \epsilon_0 E^2 = \frac{1}{2} 8.85 \times 10^{-12} \times 100^2 = 4.43 \times 10^{-8} \frac{\text{J}}{\text{m}^3}$$

$$u_m = \frac{B^2}{2\mu_0} = \frac{(0.5 \times 10^{-4})^2}{2 \times 4\pi \times 10^{-7}} = 9.95 \times 10^{-4} \frac{\text{J}}{\text{m}^3}$$

Problem H.7

A $2\ \mu\text{F}$ capacitor is given an initial charge of $6\ \mu\text{C}$ and is then connected across a $15\ \text{k}\Omega$ resistor to discharge it.

- What is the charge on the capacitor 40 ms after the resistor is connected?
- What is the current through the resistor 40 ms after it is connected?
- What is the maximum magnitude current through the resistor?

Solution to H.7

The time constant is

$$\tau = RC = 15\ \text{k}\Omega \times 2\ \mu\text{F} = 30\ \text{ms}$$

- For a discharging capacitor:

$$Q(t) = Q_0 e^{-t/\tau} = (6\ \mu\text{C}) e^{-40/30} = 1.58\ \mu\text{C}$$

- To get the current differentiate the charge.

$$I(t) = \frac{dQ}{dt} = -\frac{Q_0}{\tau} e^{-t/\tau} = -\frac{6\ \mu\text{C}}{30\ \text{ms}} e^{-40/30} = -5.27 \times 10^{-5}\ \text{A}$$

- The maximum current is at $t = 0$.

$$I_{\max} = \frac{Q_0}{\tau} = \frac{6\ \mu\text{C}}{30\ \text{ms}} = 2 \times 10^{-4}\ \text{A}$$

Problem H.8

A $2\ \text{M}\Omega$ resistor and a $3\ \mu\text{C}$ capacitor are connected across a $12\ \text{V}$ battery. What is the timeconstant of the circuit. Express the charge and currents as functions of time.

Solution to H.8

$$R = 2 \times 10^6\ \Omega, \quad C = 3 \times 10^{-6}\ \text{F} \quad \text{and} \quad \mathcal{E} = 12\ \text{V}$$

$$\tau = RC = 6\ \text{s}$$

$$Q(t) = \mathcal{E}C(1 - e^{-t/\tau}) = 36\ \mu\text{C}(1 - e^{-t/(6\ \text{s})})$$

$$I(t) = \frac{d}{dt}Q(t) = \frac{\mathcal{E}C}{RC} e^{-t/\tau} = \frac{\mathcal{E}}{R} e^{-t/\tau} = 6\ \mu\text{A} e^{-t/(6\ \text{s})}$$

Problem H.9

If a charging capacitor reaches 60% of its maximum charge after $0.90\ \text{s}$ then what is the time constant of the circuit?

Solution to H.9

$$Q(t) = Q_{\max}(1 - e^{-t/\tau}) \Rightarrow 0.6 = \frac{Q}{Q_{\max}} = (1 - e^{-t/\tau}) \Rightarrow 0.4 = e^{-t/\tau} \Rightarrow -\tau \ln 0.4 = t = 0.9 \text{ s} \Rightarrow \tau = 0.982 \text{ s}$$

Problem H.10

A 2.5 H inductor is connected in a loop circuit with a DC voltage source and a resistor. If the current increases to 90% of its final value in 3 s then what is the resistance in the circuit?

Solution to H.10

For such a circuit the current is

$$I(t) = I_{\max}(1 - e^{-t/\tau})$$

$$0.90 = \frac{I}{I_{\max}} = 1 - e^{-3/\tau} \Rightarrow e^{-3/\tau} = 0.10 \Rightarrow \tau = -\frac{3}{\ln(0.1)} = 1.3029$$

$$\tau = \frac{L}{R} = \frac{2.5}{R} \Rightarrow R = 1.92 \Omega$$

Problem H.11

An inductance L and a capacitance C both have the same time constant when combined with the same resistance.

- (a) What is the resistance and what is the value of the time constant?
 (b) If $L = 12 \text{ mH}$ and $C = 30 \mu\text{F}$ then what is R and what is the value of the time constant?

Solution to H.11

- (a) The time constants are $\tau = RC$ and $\tau = L/C$.

$$\frac{L}{R} = \tau = RC \Rightarrow R = \sqrt{\frac{L}{C}}$$

$$\tau = RC = C\sqrt{\frac{L}{C}} = \sqrt{LC}$$

- (b) Using the values $L = 12 \text{ mH}$ and $C = 30 \mu\text{F}$ gives

$$R = \sqrt{\frac{L}{C}} = \sqrt{\frac{12 \times 10^{-3}}{30 \times 10^{-6}}} = 20 \Omega \quad \text{and} \quad \tau = \sqrt{LC} = 0.6 \text{ ms.}$$

Problem H.12

A $1 \mu\text{F}$ capacitor is fully charged across a 40 V battery. It is then disconnected from the battery and connected across a 10 mH inductor. What is the maximum current through the inductor during the LC oscillations?

Solution to H.12

The initial charge on the capacitor is the maximum charge of the oscillation. It is

$$Q_{\max} = C V = 10^{-6} \times 40 = 4 \times 10^{-5} \text{ C.}$$

The angular frequency of the oscillation is

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-6} \times 0.010}} = 10^4 \frac{\text{rad}}{\text{s}}.$$

For an LC circuit the charge varies as: $Q(t) = Q_{\max} \cos(\omega t + \phi)$. The current is the derivative of the charge. $I(t) = dQ/dt = -\omega Q_{\max} \sin(\omega t + \phi)$. Since sine varies between +1 and -1 we get

$$I_{\max} = \omega Q_{\max} = 0.4 \text{ A}$$

Problem H.13

A 840 nF capacitor with an initial 105 μC is connected across a 3.30 mH inductor at $t = 0$.

- What is the energy in the capacitor at $t = 2$ ms?
- What is the energy in the inductor at $t = 2$ ms?
- What is the total energy?

Solution to H.13

For the charge as a function of time we want our sinusoidal function to be cosine since the charge has its maximum value at $t = 0$.

$$Q(t) = Q_{\max} \cos \omega t \implies I(t) = \frac{d}{dt} Q(t) = -\omega Q_{\max} \sin \omega t.$$

$$\text{where } \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3.3 \times 10^{-3} \times 840 \times 10^{-9}}} = 18993 \text{ and } Q_{\max} = Q_0 = 105 \times 10^{-6}$$

At $t = 2$ ms ,

$$Q(2 \text{ ms}) = Q_{\max} \cos(\omega \times 2 \times 10^{-3}) = 1.00683 \times 10^{-4}$$

$$I(2 \text{ ms}) = -\omega Q_{\max} \sin(\omega \times 2 \times 10^{-3}) = -0.56597$$

$$(a) U_C = \frac{Q^2}{2C} = \frac{(1.00683 \times 10^{-4})^2}{2 \times 840 \times 10^{-9}} = 6.03 \text{ mJ}$$

$$(b) U_L = \frac{1}{2} L I^2 = \frac{1}{2} 3.3 \times 10^{-3} \times 0.56597^2 = 0.529 \text{ mJ}$$

$$(c) U_{\text{total}} = \frac{Q_{\max}^2}{2C} = \frac{(105 \times 10^{-6})^2}{2 \times 840 \times 10^{-9}} = 6.56 \text{ mJ}$$

Note that $U_{\text{total}} = U_C + U_L$.