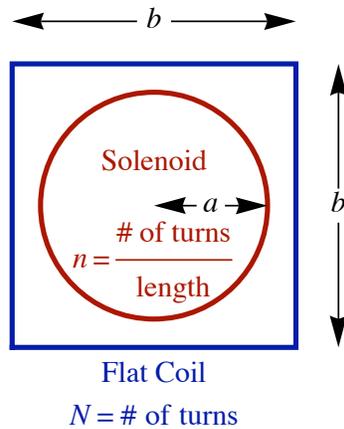


Chapter H - Problems

Blinn College - Physics 2426 - Terry Honan


Problem H.1

Refer to **Problem G.9** where a $b \times b$ square flat coil with N turns sits outside of a long solenoid with n turns per length and a circular cross-section radius a . What is the mutual inductance between the solenoid and the flat coil?



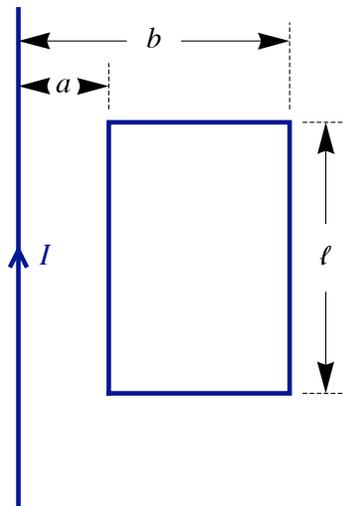Problem H.2

Refer to **Problem G.7** where we discussed a long wire next to a rectangular conduction loop. What is the mutual inductance between the long wire and the loop?



Problem H.3

What is the average induced EMF when the current through a coil with a 50 mH inductance varies from 5 A to 3 A in 0.04 s?

Problem H.4

The current through a 15 mH inductor varies as

$$I(t) = I_{\max} \sin \omega t \quad \text{where } I_{\max} = 6 \text{ A and } \omega = 200 \text{ s}^{-1}.$$

What is the EMF across the inductor as a function of time?

Problem H.5

A solenoid has 250 turns, a length of 40 cm and a diameter of 3 cm. The current through the solenoid varies as

$$I(t) = 15 t^3 - 40 t + 30 \quad (\text{in SI units}).$$

- What is the inductance of the solenoid?
- What is the voltage drop across the solenoid at $t = 2 \text{ s}$?
- What is the energy stored in the solenoid at $t = 2 \text{ s}$?

Problem H.6

A typical electric field at the earth's surface is 100 V/m and a typical magnetic field value is $5 \times 10^{-5} \text{ T}$. What are the electric and magnetic energy density, u_e and u_m .

Problem H.7

A $2 \mu\text{F}$ capacitor is given an initial charge of $6 \mu\text{C}$ and is then connected across a $15 \text{ k}\Omega$ resistor to discharge it.

- What is the charge on the capacitor 40 ms after the resistor is connected?
- What is the current through the resistor 40 ms after it is connected?
- What is the maximum magnitude current through the resistor?

Problem H.8

A $2 \text{ M}\Omega$ resistor and a $3 \mu\text{C}$ capacitor are connected across a 12 V battery. What is the timeconstant of the circuit. Express the charge and currents as functions of time.

Problem H.9

If a charging capacitor reaches 60% of its maximum charge after 0.90 s then what is the time constant of the circuit?

Problem H.10

A 2.5 H inductor is connected in a loop circuit with a DC voltage source and a resistor. If the current increases to 90% of its final value in 3 s then what is the resistance in the circuit?

Problem H.11

An inductance L and a capacitance C both have the same time constant when combined with the same resistance.

- What is the resistance and what is the value of the time constant?
- If $L = 12$ mH and $C = 30$ μ F then what is R and what is the value of the time constant?

Problem H.12

A 1 μ F capacitor is fully charged across a 40 V battery. It is then disconnected from the battery and connected across a 10 mH inductor. What is the maximum current through the inductor during the LC oscillations?

Problem H.13

A 840 nF capacitor with an initial 105 μ C is connected across a 3.30 mH inductor at $t = 0$.

- What is the energy in the capacitor at $t = 2$ ms?
- What is the energy in the inductor at $t = 2$ ms?
- What is the total energy?